

**Dhaka International University**  
**Department of Computer Science and Engineering**




**PHY-104: Electricity and Magnetism Lab**

**Experiment 3**

**To investigate the characteristics of a series DC circuit and to verify  
Kirchoff's Voltage Law (KVL)**

---

**OBJECTIVES**

-  To investigate circuits with resistors connected in series.
-  To verify Kirchoff's Voltage Law (KVL).
-  To verify Voltage Divider Rule (VDR).

## THEORY

### Series Circuit:

Figure. 1 shows three resistors,  $R_1$ ,  $R_2$ , and  $R_3$ , connected in series in a closed circuit powered by a single battery or emf source. In this circuit the current supplied by the battery flows through each resistor, with the current in each resistor being the same. If the current supplied by the battery is  $I_T$ , the current in each resistor is  $I_1$ ,  $I_2$ , and  $I_3$ , and they are all one and the same, then  $I_T = I_1 = I_2 = I_3$ .

The voltage drop across the battery  $V_T$  will be the total sum of the individual drops across each of the 3 resistors, and

$$V_T = V_1 + V_2 + V_3$$

where  $V_1$  is the potential difference across  $R_1$ ,  $V_2$  is the potential difference across  $R_2$ , and  $V_3$  is the potential difference across  $R_3$ . By using Ohm's law

$$V_T = I_T \times R_T$$

$$V_1 = I_1 \times R_1$$

$$V_2 = I_2 \times R_2$$

And

$$V_3 = I_3 \times R_3$$

Finally,

$$I_T R_T = I_1 R_1 + I_2 R_2 + I_3 R_3$$

and since  $I_T = I_1 = I_2 = I_3$

$$R_T = R_1 + R_2 + R_3$$

Therefore, when resistors are connected in series, the total resistance is just the sum of the individual resistances. While this has been shown for 3 resistors, the total resistance of any number  $N$  ( $N \geq 2$ ) of resistors connected in series, end to end, can be found using the same general procedure. Therefore, for resistors connected in series

$$R_T = \sum_{i=1}^N R_i$$

### **Kirchoff's Voltage law (KVL):**

We can state Kirchhoff's Voltage Law in three ways which all really say the same thing.

- The algebraic sum of the voltage drops around any closed path of an electric circuit equal zero.
- The algebraic sum of the voltage rises around any closed path of an electric circuit equal zero
- The algebraic sum of the voltage rises equal the algebraic sum of the voltage drops around any closed path of an electric circuit.

Applying Kirchoff's voltage Law around closed loop of Figure 1., we find

$$V_T = V_1 + V_2 + V_3$$

Where,  $V_1 = IR_1$ ,  $V_2 = IR_2$ ,  $V_3 = IR_3$

Current I is same throughout the circuit for figure 1. The Current is calculated by using Ohm's Law,

$$I = \frac{V_T}{R_T}$$

The voltage divider rule states that the voltage across an element or across series combination of elements in a series circuit is equal to the resistance of the element divided by total resistance of the series circuit and multiplied by the total impressed voltage. For the elements of Figure 1.

$$V_1 = \frac{R_1 E}{R_T}, \quad V_2 = \frac{R_2 E}{R_T}, \quad V_3 = \frac{R_3 E}{R_T}$$

### **EQUIPMENTS**

- Variable DC power supply
- Digital Multimeter
- Resistances- 3 pieces
- Trainer Board
- Connecting wires

## CIRCUIT DIAGRAM

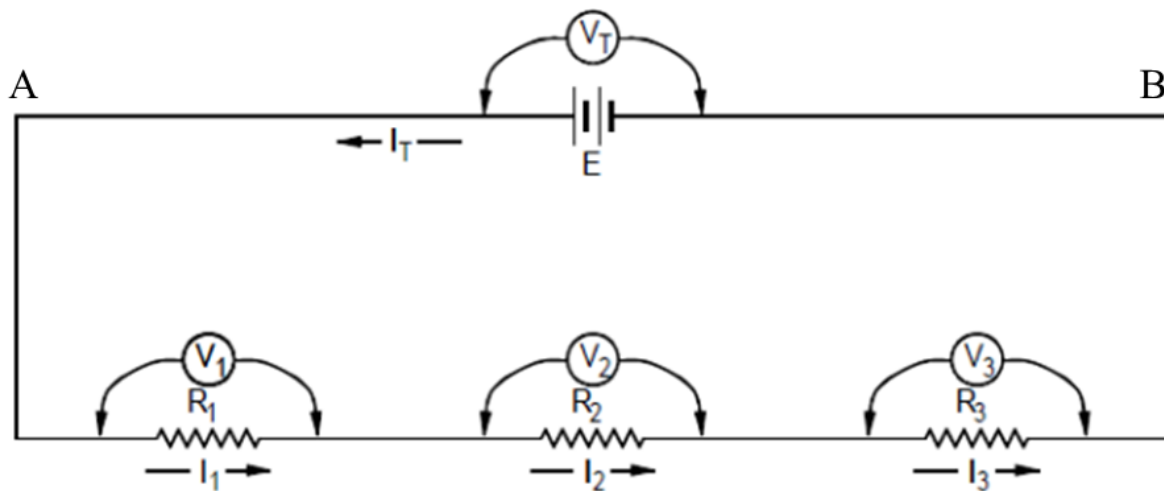


Figure 1: Three resistors  $R_1$ ,  $R_2$ , and  $R_3$  connected in series.

## PROCEDURE

1. Measure the resistances by using Ohmmeter and record the values in Table 1.
2. Construct the circuit as shown in Figure 1.
3. Then measure input resistance  $R_T$  across points A-B using Ohmmeter and record that value in Table 1.
4. Turn on the DC power supply and set the DC supply to 20V by using Voltmeter.
5. Measure voltage across each resistor with Voltmeter and record in the Table 1.
6. Calculate  $V_1$ ,  $V_2$ ,  $V_3$  using Voltage Divider Rule (VDR).

## EXPERIMENTAL DATA

Table 1:

Nominal values of Resistance ( $\Omega$ )	Measured values of Resistance by Ohmmeter ( $\Omega$ )	Equivalent Resistance, $R_T$		Measured voltage across each resistor (V)	Calculated Voltage using VDR (V)
		Measured $R_T$ by using Ohmmeter ( $\Omega$ )	Calculated $R_T = R_1 + R_2 + R_3$ ( $\Omega$ )		
$R_1 =$				$V_1 =$	
$R_2 =$				$V_2 =$	
$R_3 =$				$V_3 =$	

## **CALCULATION**

## **CONCLUSION**

From the above experiment it we have studied and verified that the observation value is approximately same to the calculation value in series circuit.