

Problem-01: Find the source voltage, the voltage v_1 , and current I_L for the circuit in fig.

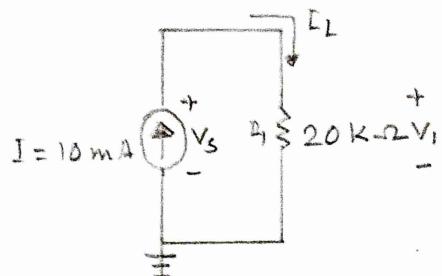


Fig:

Solⁿ: Given,

$$I = I_L = 10 \text{ mA}$$


$$R_1 = 20 \text{ k}\Omega$$

$$\therefore v_s = v_1 = I R_1 = (10 \times 20) \text{ V} = 200 \text{ V}$$

\therefore Source voltage = Voltage, $v_1 = 200 \text{ V}$

(Ans.)

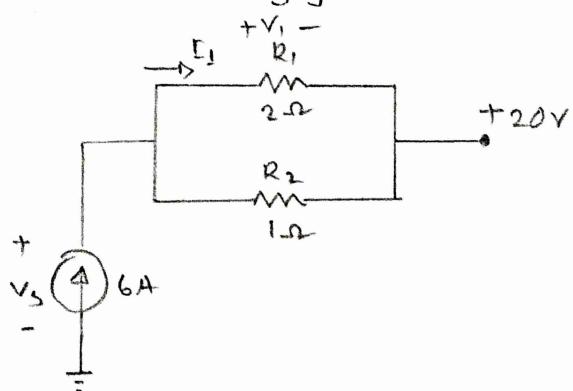Problem-02: Determine the current I_L and the voltage v_s for the network in fig.



Solⁿ: Given,

$$R_1 = 2 \Omega, R_2 = 1 \Omega$$

$$\therefore R_T = \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} = \frac{2}{3} \Omega$$

$$I = 6 \text{ A}$$

As CDR,

$$I_1 = \frac{R_T}{R_1} \cdot I = \frac{\frac{2}{3}}{2} \times 6 = 2 \text{ A}$$


$$\therefore \text{voltage } v_1 = I_1 R_1 = 2 \times 2 = 4 \text{ V}$$

As KVL,

$$V_s = v_1 + 20 \text{ V} = 4 + 20 = 24 \text{ V}$$


(Ans)

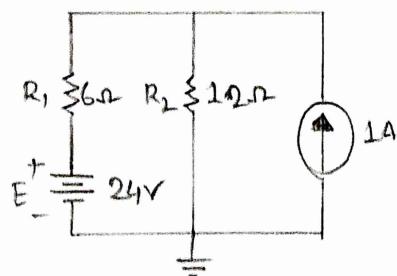Q3 Problem - 03: Determine the node voltages for the network in Fig and calculate the current flow through $6\text{-}\Omega$ and $12\text{-}\Omega$ resistors.



Fig

Sol'n:

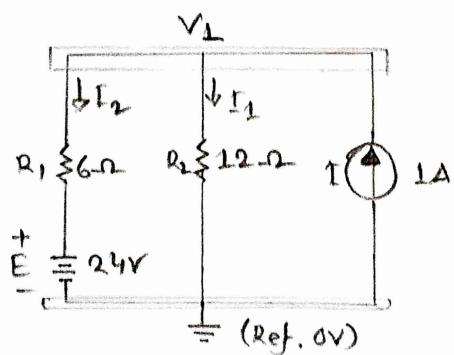

Applying KCL at node v_1 ,

$$\frac{v_1 - 24}{6} + \frac{v_1 - 0}{12} - 1 = 0$$

$$\Rightarrow 2V_1 - 48 + V_1 - 12 = 0$$

$$\Rightarrow 3V_1 = 60$$


$$\therefore V_1 = 20$$

$$\therefore I_1 = \frac{V_1 - 24V}{6\Omega} = \frac{20V - 24V}{6\Omega} = -0.67 A$$

$$\therefore I_2 = \frac{V_1 - 0}{12\Omega} = \frac{20}{12} = 1.67 A$$

(Ans)

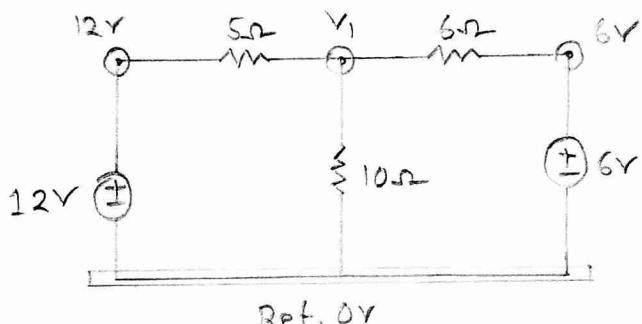Problem-04: Determine the current through 10Ω resistor using nodal analysis.



Fig

Applying KCL at node V_1 ,

$$\frac{V_1 - 12}{5} + \frac{V_1 - 0}{10} + \frac{V_1 - 6}{6} = 0$$

$$\Rightarrow 2V_1 - 24 + V_1 + \frac{10V_1 - 60}{6} = 0$$

$$\Rightarrow 18V_1 - 144 + 10V_1 - 60 = 0$$

$$\Rightarrow V_1 = \frac{204}{28} = 7.28 V$$

$$\therefore I_{10\Omega} = \frac{V_1 - 0}{10\Omega} = \frac{7.28V}{10\Omega} = 0.728 A.$$

(Ans)

Problem - 05: Determine the node voltage of the network fig. and calculate the current flow through 8Ω , 4Ω and 10Ω resistor.

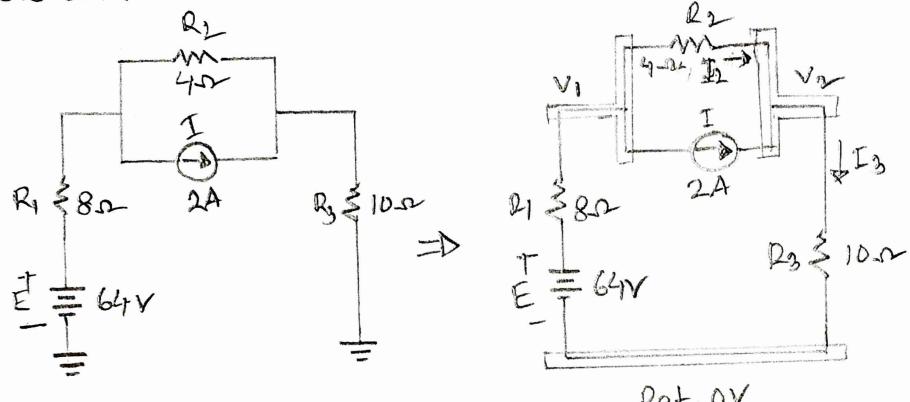


Fig: 05

Sol:

Apply KCL at node V_1 ,

$$\frac{V_1 - 64}{8} + \frac{V_1 - V_2}{4} + 2 = 0$$

$$\Rightarrow V_1 - 64 + 2V_1 - 2V_2 + 16 = 0$$

$$\Rightarrow 3V_1 - 2V_2 - 48 = 0 \quad \text{--- (1)}$$

Apply KCL at node V_2 ,

$$\frac{V_2 - 0}{10} + \frac{V_2 - V_1}{4} - 2 = 0$$

$$\Rightarrow 2V_2 + 5V_2 - 5V_1 - 40 = 0$$

$$\Rightarrow -5V_1 + 7V_2 - 40 = 0 \quad \text{--- (2)}$$

$$\{(1 \times 5) + (2 \times 3)\} \Rightarrow 15V_1 - 10V_2 - 240 - 15V_1 + 21V_2 - 120 = 0$$

$$\Rightarrow 11V_2 = 360$$

$$\therefore V_2 = 32.73 \text{ V}$$

$$\therefore V_1 = (2V_2 + 48)/3 = (2 \times 32.73 + 48)/3 = 37.82 \text{ V}$$

$$\therefore \text{Current flow through } 8\Omega \text{ resistor, } I_{R_1} = \frac{V_1 - 64}{8}$$

$$= \frac{37.82 - 64}{8}$$

$$= -3.27 A$$

$$\therefore \text{Current flow through } 4\Omega \text{ resistor, } I_{R_2} = \frac{V_1 - V_2}{4}$$

$$= \frac{37.82 - 32.73}{4}$$


$$= 1.27 A$$

$$\therefore \text{Current flow through } 10\Omega \text{ resistor, } I_{R_3} = \frac{V_2 - 0}{10}$$

$$= \frac{32.73}{10} = 3.27 A$$

(Ans.)

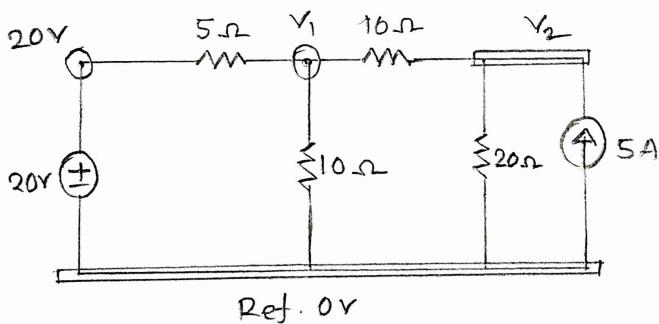Problem-06: Find the node voltage in the following circuit and determine the current flow through 20Ω resistor.



Solⁿ:

Apply KCL at node V_1 ,

$$\frac{V_1 - 20}{5} + \frac{V_1 - 0}{10} + \frac{V_1 - V_2}{10} = 0$$

$$\Rightarrow 2V_1 - 40 + V_1 + V_1 - V_2 = 0$$

$$\Rightarrow 4v_1 - v_2 = 40 \quad \text{--- (1)}$$

Apply KCL at node v_2 ,

$$\frac{v_2 - v_1}{10} + \frac{v_2 - 0}{20} - 5 = 0$$

$$\Rightarrow 2v_2 - 2v_1 + v_2 - 100 = 0$$

$$\Rightarrow -2v_1 + 3v_2 = 100 \quad \text{--- (11)}$$

$$\{(1) + 2 \times (11)\} \Rightarrow 4v_1 - v_2 - 4v_1 + 6v_2 = 40 + 200$$

$$\Rightarrow 5v_2 = 240$$


$$\therefore v_2 = 48V$$

$$\therefore v_1 = (40 + v_2)/4 = (40 + 48)/4 = 22V$$

current flow through 20Ω resistor, $I_{20\Omega} = \frac{v_2 - 0}{20\Omega} = \frac{48V}{20\Omega} = 2.4A$.

(Ans.)

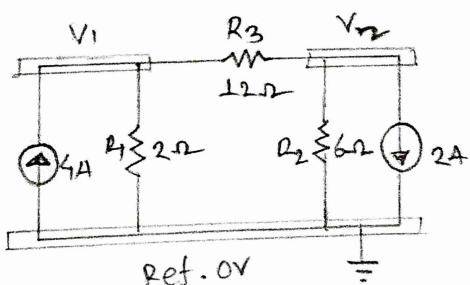Problem-07: Determine the nodal voltages for the network shown below.



Solⁿ: Apply KCL at node v_1

$$-4 + \frac{v_1 - 0}{2} + \frac{v_1 - v_2}{12} = 0$$

$$\Rightarrow -48 + 6v_1 + v_1 - v_2 = 0$$

$$\Rightarrow 7v_1 - v_2 = 48 \quad \text{--- (1)}$$

Apply KCL at node v_2 ,

$$\frac{v_2 - v_1}{12} + \frac{v_2 - 0}{6} + 2 = 0$$

$$\Rightarrow v_2 - v_1 + 2v_2 + 24 = 0$$

$$\Rightarrow 3v_2 - v_1 = -24 \quad \text{--- (2)}$$

$$\{(1) \times 3 + (2)\} \Rightarrow 21v_1 - 3v_2 + 3v_2 - v_1 = 144 - 24$$


$$\Rightarrow 20v_1 = 120$$

$$\therefore v_1 = 6 \text{ V}$$

$$\therefore v_2 = 7v_1 - 48 = 42 - 48 = -6 \text{ V}$$

(Ans.)

Problem-08: Determine the node voltages in the following circuit shown below.

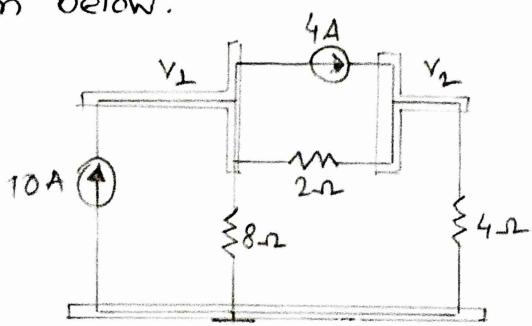

Ref. 0V

Apply KCL at node v_1 ,

$$-10 + 4 + \frac{v_1 - v_2}{2} + \frac{v_1 - 0}{8} = 0$$

$$\Rightarrow -48 + v_1 + 4v_1 - 4v_2 = 0$$

$$\Rightarrow 5v_1 - 4v_2 = 48 \dots \dots \dots \textcircled{1}$$

Apply KCL at node v_2 ,

$$-4 + \frac{v_2 - v_1}{2} + \frac{v_2 - 0}{4} = 0$$

$$\Rightarrow -16 + 2v_2 - 2v_1 + v_2 = 0$$

$$\Rightarrow -2v_1 + 3v_2 = 16 \dots \dots \textcircled{11}$$

$$\left\{ \textcircled{1} \times 2 + \textcircled{11} \times 5 \right\} \Rightarrow 10v_1 - 8v_2 - 10v_1 + 15v_2 = 96 + 80$$


$$\Rightarrow 7v_2 = 176$$

$$\therefore v_2 = 25.14$$

$$\therefore v_1 = (48 + 4v_2) / 5 = (48 + 4 \times 25.14) / 5 = 29.71 \text{ V}$$

(Ans.)

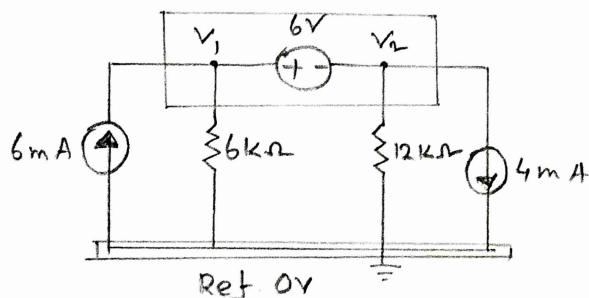Problem-09: Determine the current I_o in the network shown below.



Soln: Apply KCL at supernode

$$-6 + \frac{v_1 - 0}{6} + 4 + \frac{v_2 - 0}{12} = 0$$

$$\Rightarrow 2v_1 + v_2 - 24 = 0$$

$$\Rightarrow 2v_1 + v_2 = 24 \quad \text{--- } \textcircled{1}$$

$$V_1 - V_2 = 6 \quad \text{--- (1)}$$

$$\{ (1) + (1) \} \Rightarrow 2V_1 + V_2 + V_1 - V_2 = 24 + 6$$

$$\Rightarrow 3V_1 = 30$$

$$\Rightarrow V_1 = 10$$


$$\therefore V_2 = V_1 - 6 = 10 - 6 = 4$$

\therefore current flow through $6\text{k}\Omega$ resistor, $I_{6\text{k}\Omega} = \frac{V_1 - 0}{6\text{k}\Omega} = \frac{10\text{V}}{6\text{k}\Omega} = 1.67\text{mA}$

\therefore current flow through $12\text{k}\Omega$ resistor, $I_{12\text{k}\Omega} = \frac{V_2 - 0}{12\text{k}\Omega} = \frac{4}{12} = 0.33\text{mA}$

(Ans.)

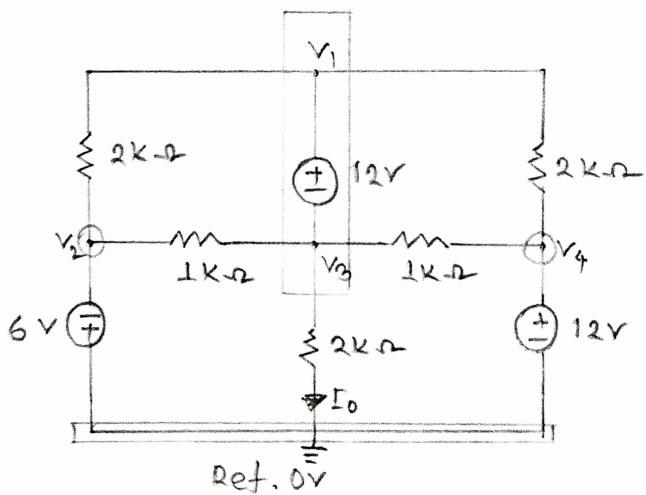■ Problem 40: Determine the current I_o in the network in the circuit shown below.



Solⁿ:

From the circuit we can determine,

$$V_2 = -6\text{V}$$

$$V_4 = 12\text{V}$$

Apply KCL at supernode

$$\frac{V_3 - V_2}{1} + \frac{V_3 - 0}{2} + \frac{V_3 - V_4}{1} + \frac{V_1 - V_2}{2} + \frac{V_1 - V_4}{2} = 0$$

$$\Rightarrow V_3 + 6 + \frac{V_3}{2} + V_3 - 12 + \frac{V_1 + 6}{2} + \frac{V_1 - 12}{2} = 0$$

$$\Rightarrow 2V_3 + 12 + V_3 + 2V_3 - 24 + V_1 + 6 + V_1 - 12 = 0$$

$$\Rightarrow 2V_1 + 5V_3 = 18 \quad \text{--- (1)}$$

$$V_1 - V_3 = 12 \quad \text{--- (2)}$$

$$\left\{ (1) - (2) \times 2 \right\} \Rightarrow 2V_1 + 5V_3 - 2V_1 + 2V_3 = 18 - 24$$


$$\Rightarrow 7V_1 = -6$$

$$\therefore V_1 = -0.857 \text{ V}$$

$$\begin{aligned} \text{Current flow, } I_0 &= \frac{V_3 - 0}{2k\Omega} \\ &= -\frac{0.857 \text{ V}}{2k\Omega} = -0.4285 \text{ mA.} \end{aligned}$$

(Ans)

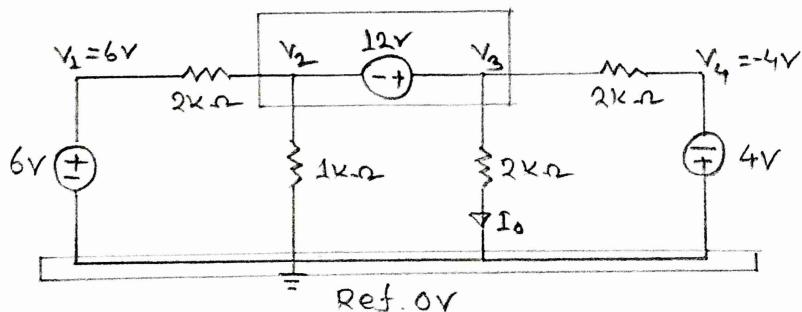Problem : 11 - Use nodal analysis to find I_0 in the network in the figure below.



Applying KCL at supernode

$$\frac{V_2 - 6}{2} + \frac{V_2 - 0}{1} + \frac{V_3 + 4}{2} + \frac{V_3 - 0}{2} = 0$$

$$\Rightarrow V_2 - 6 + 2V_2 + V_3 + 4 + V_3 = 0$$

$$\therefore 2v_3 + 3v_2 = 2 \quad \text{--- (1)}$$

$$v_3 - v_2 = 12 \quad \text{--- (2)}$$

$$\left\{ \begin{array}{l} (1) \\ (2) \end{array} \right. \times 3 \Rightarrow 2v_3 + 3v_2 + 3v_3 - 3v_2 = 2 + 36$$

$$\therefore 5v_3 = 38$$


$$\therefore v_3 = 7.6$$

$$\therefore v_2 = -4.4$$

$$\therefore I_0 = \frac{v_3 - 0}{2} = \frac{7.6 - 0}{2} = 3.8 \text{ mA}$$

(Ans.)

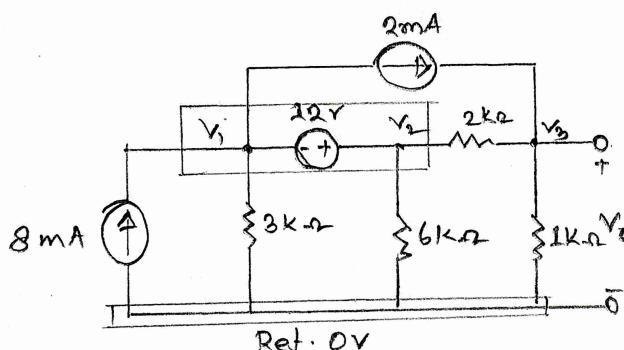Q) Problem: 12 - Find v_o in figure below using nodal analysis.



Soln:

Applying KCL at supernode.

$$-8 + \frac{v_1 - 0}{3} + 2 + \frac{v_2 - v_3}{2} + \frac{v_2 - 0}{6} = 0$$

$$\therefore -36 + 2v_1 + 3v_2 - 3v_3 + v_2 = 0$$

$$\therefore 2v_1 + 4v_2 - 3v_3 = 36 \quad \text{--- (1)}$$

$$v_2 - v_3 = 12 \quad \text{--- (2)}$$

$$\therefore v_2 = 12 + v_3 \quad \text{--- (4)}$$

Applying KCL at node v_3 ,

$$\frac{v_3 - v_2}{2} + \frac{v_3 - 0}{1} - 2 = 0$$

$$\Rightarrow v_3 - v_2 + 2v_3 = 4$$

$$\Rightarrow 3v_3 - v_2 = 4 \quad \text{--- (3)}$$

$$\Rightarrow 3v_3 - (12 + v_1) = 4 \quad [\text{From eqn. (4)}]$$

$$\Rightarrow 3v_3 - 12 - v_1 = 4$$

$$\Rightarrow 3v_3 = 16 + v_1 \quad \text{--- (5)}$$

$$\therefore 2v_1 + 4v_2 - 2v_3 = 36$$

$$\Rightarrow 2v_1 + 4(12 + v_1) - (16 + v_1) = 36$$

$$\Rightarrow 2v_1 + 48 + 4v_1 - 16 - v_1 = 36$$

$$\Rightarrow 5v_1 = 4$$

$$\therefore v_1 = \frac{4}{5} = 0.8V$$


$$\therefore v_3 = (16 + v_1)/3$$

$$\therefore (16 + 0.8)/3 = 5.6V$$

$$\therefore v_2 = 12 + v_1 = 12.8V$$

(Ans.)

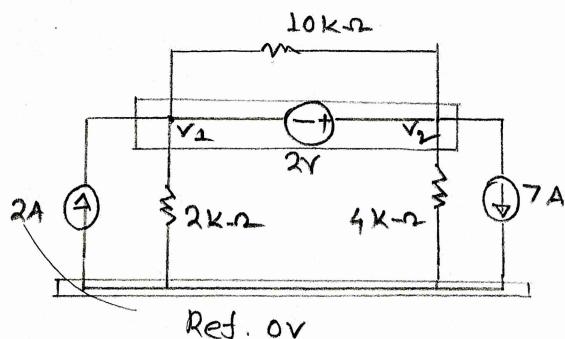Problem-13: For the circuit shown below find the node voltage.



Applying KCL at supernode

$$-2 + \frac{v_1 - 0}{2} + \frac{v_2 - 0}{4} + 7 = 0$$

$$\Rightarrow -8 + 2v_1 + v_2 + 28 = 0$$

$$\Rightarrow 2v_1 + v_2 = -20 \quad \text{--- (1)}$$

$$v_2 - v_1 = 2 \quad \text{--- (2)}$$

$$\{(1) - (2)\} \Rightarrow 2v_1 + v_2 - v_2 + v_1 = -20 - 2$$


$$\Rightarrow 3v_1 = -22$$

$$\therefore v_1 = -22/3 = -7.33 \text{ V}$$

$$\therefore v_2 = 2 + v_1 = 2 - 7.33 = -5.33 \text{ V}$$

(Ans.)

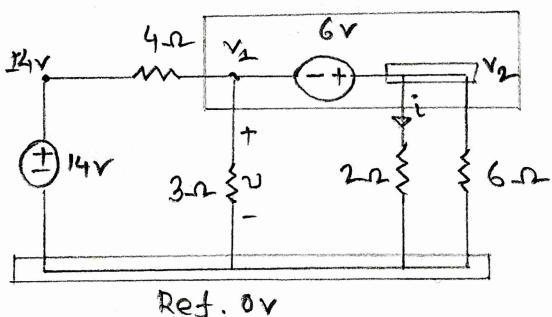■ Problem - 14: Find v and i in the circuit below.



Solⁿ:

Applying KCL at supernode

$$\frac{v_1 - 14}{4} + \frac{v_1 - 0}{3} + \frac{v_2 - 0}{2} + \frac{v_2 - 0}{6} = 0$$

$$\Rightarrow \frac{6v_1 - 84}{4} + 2v_1 + 3v_2 + v_2 = 0$$

$$\Rightarrow 6v_1 - 84 + 8v_1 + 16v_2 = 0$$

$$\Rightarrow 7v_1 + 8v_2 = 42 \quad \text{--- } ①$$

$$v_2 - v_1 = 6 \quad \text{--- } ②$$

$$\left. \begin{array}{l} \left\{ ① + ② \times 7 \right\} \Rightarrow 7v_1 + 8v_2 + 7v_2 - 7v_1 = 42 + 42 \\ \Rightarrow 15v_2 = 84 \end{array} \right.$$


$$\therefore v_2 = 5.6 \text{ V}$$

$$\therefore v_1 = 5.6 - 6 = -0.4 \text{ V}$$

$$\therefore v = v_1 = -0.4 \text{ V}$$

$$\therefore i = \frac{v_2 - 0}{2} = \frac{5.6 - 0}{2} = 2.8 \text{ mA} \quad (\text{Ans.})$$

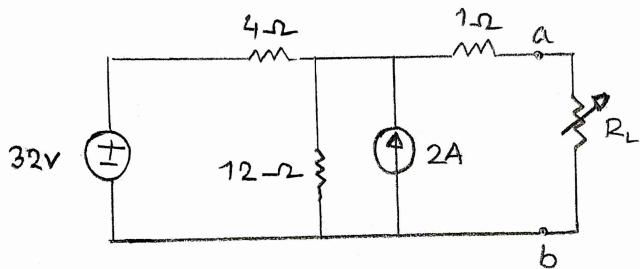Problem: 15 - Find the thevenin equivalent circuit of the circuit shown in the figure below, to the left of the terminal. Then find the current through $R_L = 6\Omega, 16\Omega, 36\Omega$



501ⁿ:

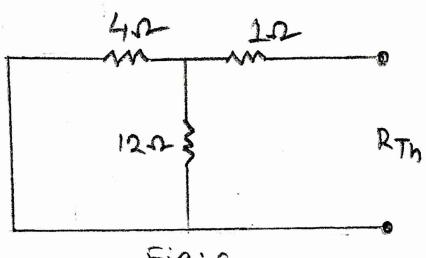


Fig:a

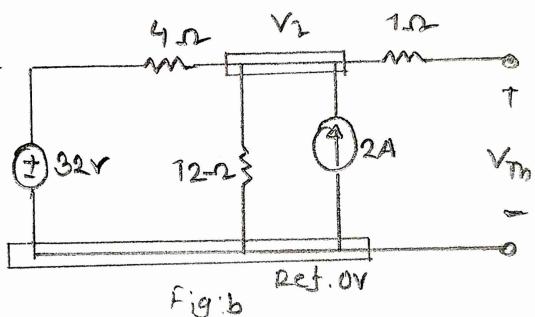


Fig. b Ref. ov

Find R_{Th} ,

We find by turning off the 32V voltage source (replacing it with a short circuit) and the 2-A current source (replacing it with an open circuit). The circuit becomes as fig:a.

$$\therefore R_{Th} = (4\Omega \parallel 12\Omega) + 1\Omega$$

$$= \left(\frac{1}{4} + \frac{1}{12}\right)^{-1} + 1 = 4\Omega$$

Find V_{TH} ,

Applying KCL at node v_1 in fig:b,

$$\frac{v_1 - 32}{4} + \frac{v_1 - 0}{12} - 2 = 0$$


$$= 0 \quad 3v_1 - 96 + v_1 - 24 = 0$$

$$\Rightarrow 4r_1 = 120$$

$$\therefore V_1 = 30 \text{ V}$$

$$\therefore V_1 = V_{Th} = 30V$$

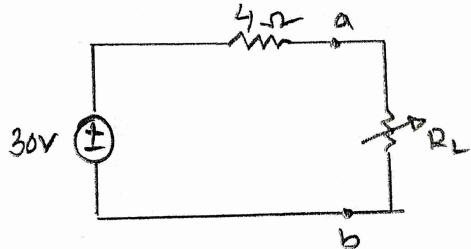\therefore Thevenin equivalent circuit in fig: c



$$\begin{aligned}\text{The current through } R_L \text{ is } \therefore I_L &= \frac{V_{Th}}{R_{Th} + R_L} \\ &= \frac{30}{4 + R_L}\end{aligned}$$


$$\therefore \text{when } R_L = 6\Omega, I_L = \frac{30}{4+6} = 3A$$

$$\therefore \text{when } R_L = 16\Omega, I_L = \frac{30}{4+16} = 1.5A$$

$$\therefore \text{when } R_L = 36\Omega, I_L = \frac{30}{4+36} = 0.75A$$

(Ans.)

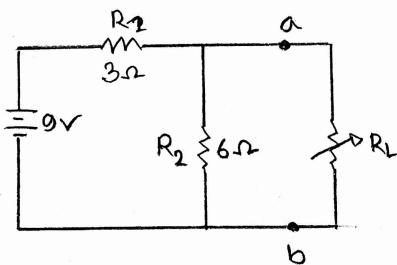Problem-16: Find the thevenin equivalent circuit for the network below in figure. Determine the current through R_L for values of $2\Omega, 10\Omega, 100\Omega$



Find R_{Th} ,

We find by turning off the 9V voltage source, replacing it with a short-circuit. The circuit becomes as fig:a.

$$\therefore R_{Th} = (3\Omega || 6\Omega) = 2\Omega$$


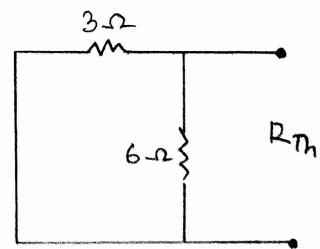


Fig: a

Find. E_{Th} ,

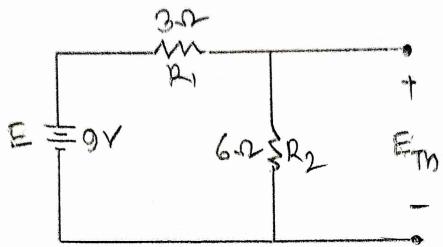

∴ Open circuit voltage E_{Th} is same as voltage drop across the 6Ω resistor.

∴ Applying VDR,

$$\begin{aligned} E_{Th} &= \frac{R_2}{R_T} \cdot V \\ &= \frac{R_2}{R_1 + R_2} \cdot V = \frac{6}{9} \cdot 9 = 6V \end{aligned}$$

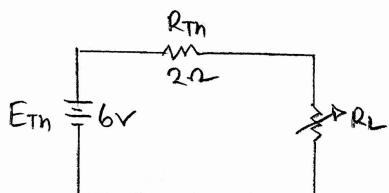


fig: b

Thevenin equivalent circuit in fig : b

$$\begin{aligned} \text{The current through } R_L \text{ is } I_L &= \frac{E_{Th}}{R_{Th} + R_L} \\ &= \frac{6}{2 + R_L} \end{aligned}$$


$$\therefore \text{when } R_L \text{ is } 2\Omega, I_L = \frac{6}{2+2} = 1.5A$$

$$\therefore \text{when } R_L \text{ is } 10\Omega, I_L = \frac{6}{2+10} = 0.5A$$

$$\therefore \text{when } R_L \text{ is } 100\Omega, I_L = \frac{6}{2+100} = 0.06A$$


(Ans.)

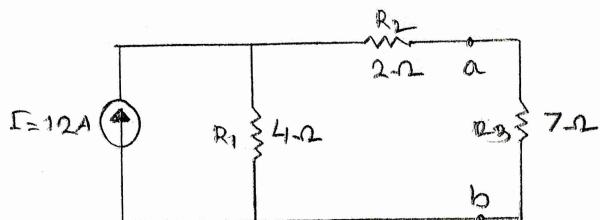Prob12: Find the Thevenin equivalent circuit and determine the current flow through R_L in the figure below.



Soln: Find R_{Th} ,

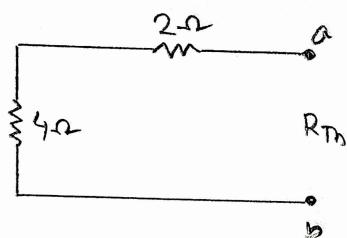
We find by turning off the current source (12A) replacing with an open circuit.



$$\therefore R_{Th} = 2\Omega + 4\Omega = 6\Omega$$


Find V_{Th} .

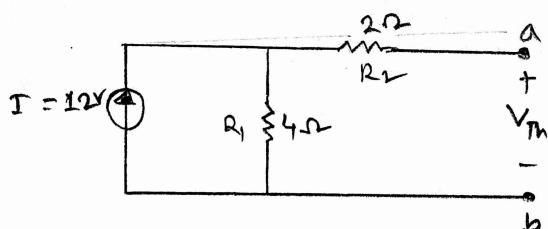Open circuit voltage V_{Th} is same as voltage drop in 4Ω resistor



$$\therefore V_{Th} = IR_1 = 12 \times 4 = 48V$$

∴ Thevenin equivalent circuit.

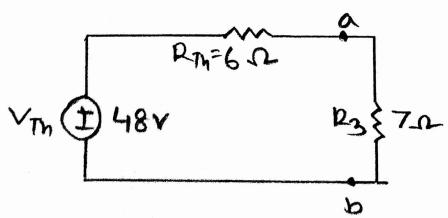


∴ Current through R_L is

$$I_L = \frac{V_{Th}}{R_{Th} + R_L}$$

$$= \frac{48}{6+7} = 3.69A$$

(Ans)

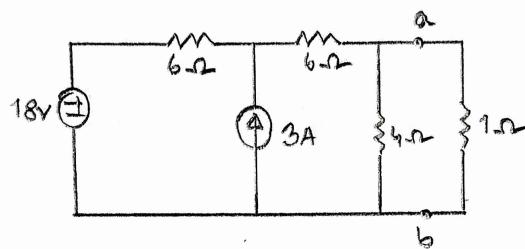Problem - 18 : Determine the thevenin equivalent circuit at terminal a-b. Find the current flow through 1Ω resistor.



Soln:

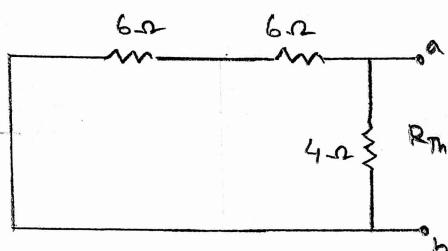


fig: (a)

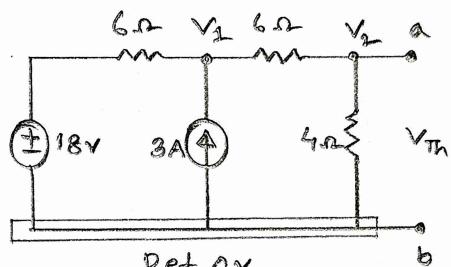


fig: (b)

Find R_{Th} ,

$$\therefore R_{Th} = (6\Omega + 6\Omega) \parallel 4\Omega = 3\Omega$$

Find V_{Th} ,

Apply KCL at node v_1 in fig : (b)

$$\frac{v_1 - 18}{6} - 3 + \frac{v_1 - v_2}{6} = 0$$

$$\Rightarrow v_1 - 18 - 18 + v_1 - v_2 = 0$$

$$\Rightarrow 2v_1 - v_2 = 36 \quad \text{--- (1)}$$

Apply KCL at node v_2 in fig (b);

$$\frac{v_2 - v_1}{6} + \frac{v_2 - 0}{4} = 0$$

$$\Rightarrow 2v_2 - 2v_1 + 3v_2 = 0$$

$$\Rightarrow -2v_1 + 5v_2 = 0 \quad \text{--- (2)}$$

\therefore Solving equation (1) and (2),

$$V_1 = 22.5V$$

$$V_2 = 9V$$

$$\therefore V_{Th} = V_2 - 0 = 9 - 0 = 9V$$

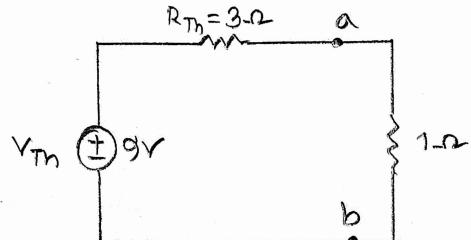


Fig: c


Thevenin equivalent circuit in fig: c

$$\therefore \text{current through } R_L \text{ is, } I_L = \frac{V_{Th}}{R_{Th} + R_L}$$

$$= \frac{9}{3+1}$$

$$\text{when } R_L = 1\Omega, I_L = \frac{9}{3+1} = 2.25A$$

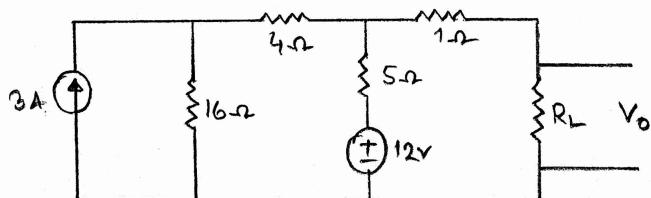■ Problem: 19 - Apply Thevenin theorem to find V_o when $R_L = 10\Omega$



Sol'n:

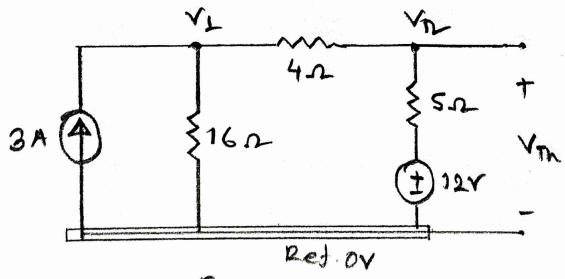


Fig: a

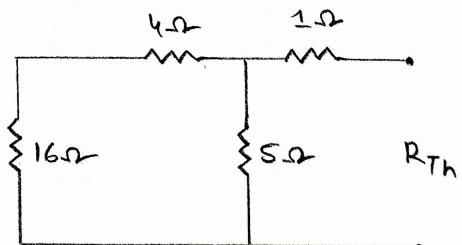


Fig: b

Find V_{Th} : (fig: a)

Applying KCL at node v_1 ,

$$-3 + \frac{v_1 - 0}{16} + \frac{v_1 - v_2}{4} = 0$$

$$\Rightarrow -48 + v_1 + 4v_1 - 4v_2 = 0$$

$$\Rightarrow 5v_1 - 4v_2 = 48 \quad \text{--- (1)}$$

Applying KCL at node v_2 ,

$$\frac{v_2 - v_1}{4} + \frac{v_2 - 12}{5} = 0$$

$$\Rightarrow 5v_2 - 5v_1 + 4v_2 - 48 = 0$$

$$\Rightarrow -5v_1 + 9v_2 = 48 \quad \text{--- (2)}$$

By solving equation (1) and (2)

$$v_1 = 24.96 \text{ V}$$

$$v_2 = 19.2 \text{ V}$$

$$\therefore V_{Th} = v_2 - 0 = 19.2 - 0 = 19.2 \text{ V}$$

Find R_{Th} : (fig-b)

$$R_{Th} = ((4\Omega || 16\Omega) || 5\Omega) + 1\Omega$$

$$= 5\Omega$$


for $R_L = 10\Omega$,

$$\therefore V_o = \frac{R_L}{R_{Th} + R_L} \cdot V_{Th}$$

$$= \frac{10}{5+10} \cdot 19.2 \text{ V}$$

$$= 12.8 \text{ V}$$

(Ans.)

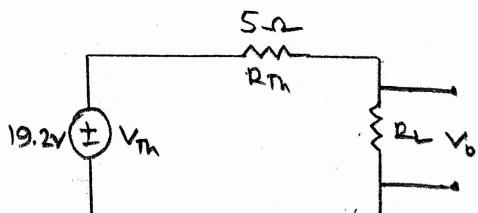

Problem - 20 : Design the thevenin equivalent circuit at terminal a-b for the circuit shown below.

Sol:

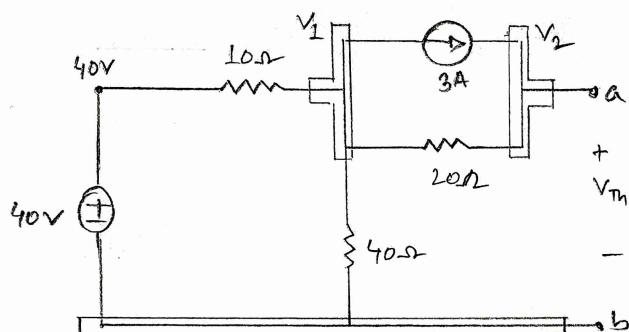
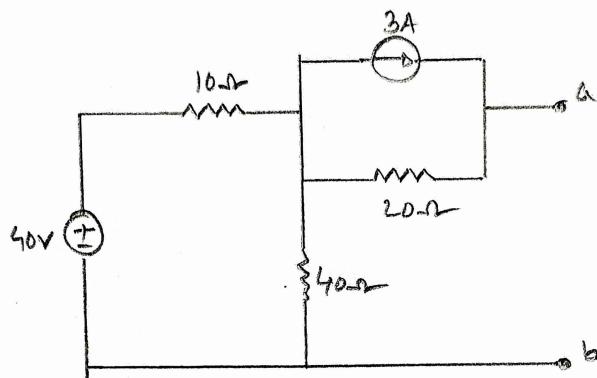


Fig: a

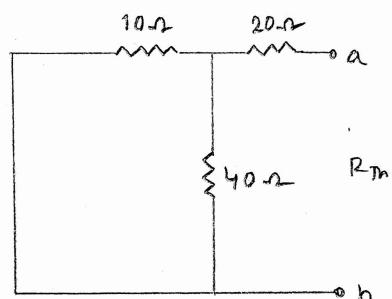


Fig: b

Find V_{Th} : (Fig-a)

Applying KCL at node v_1 ,

$$\frac{v_1 - 0}{40} + \frac{v_1 - 40}{10} + \frac{v_1 - v_2}{20} + 3 = 0$$

$$\Rightarrow v_1 - 4v_1 - 160 + 2v_1 - 2v_2 + 120 = 0$$

$$\Rightarrow 7v_1 - 2v_2 = 40 \quad \text{--- (1)}$$

Applying KCL at node v_2 ,

$$\frac{v_2 - v_1}{20} - 3 = 0$$

$$\Rightarrow v_2 - v_1 - 60 = 0$$

$$\Rightarrow -v_1 + v_2 = 60 \quad \text{--- (2)}$$

By solving equation ① and ②;

$$V_1 = 32V$$

$$V_2 = 92V$$

$$\therefore V_{Th} = V_2 - 0 = 92V - 0 = 92V$$

Find R_{Th} (Fig : b)

$$R_{Th} = (10\Omega \parallel 40\Omega) + 20\Omega$$

$$= 8\Omega + 20\Omega = 28\Omega$$


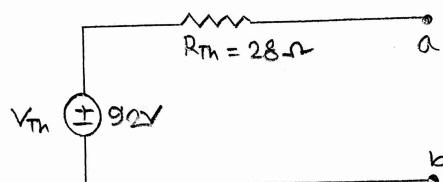


Fig: Thevenine Equivalent Circuit

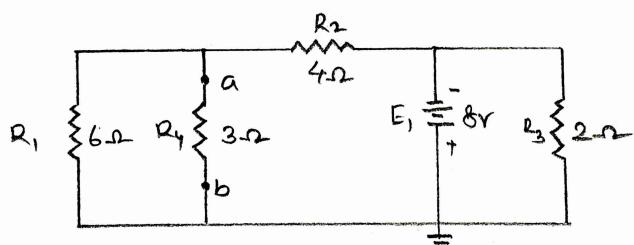~~Q~~ Problem : 21 - Find the thevenin equivalent circuit at terminal a-b for the network shown in Figure below.



Soln:

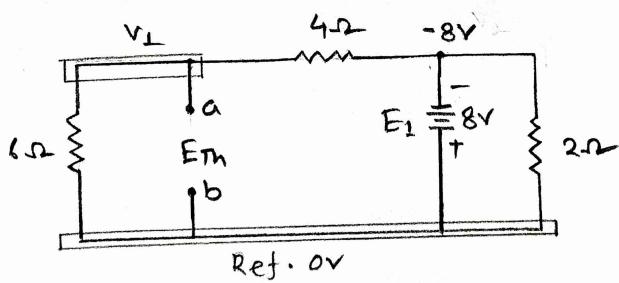


Fig: a

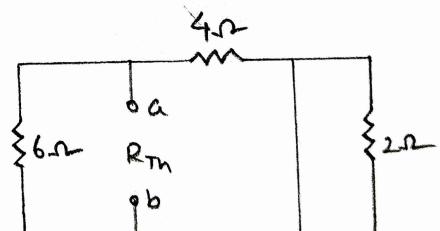


fig: b

Find E_{Th} (Fig:a)

Applying KCL at node v_1 ,

$$\frac{v_1 - 0}{6} + \frac{v_1 + 8}{4} = 0$$

$$\therefore 2v_1 + 3v_1 + 24 = 0$$

$$\therefore 5v_1 = -24$$


$$\therefore v_1 = -4.8 \text{ V}$$

$$\therefore E_{Th} = (v_1 - 0)v = (-4.8 \text{ V} - 0 \text{ V}) = -4.8 \text{ V}$$


Find R_{Th} (Fig:b)

$$R_{Th} = 4\Omega \parallel 6\Omega$$
$$= 2.4\Omega$$

\therefore Thevenin equivalent circuit:

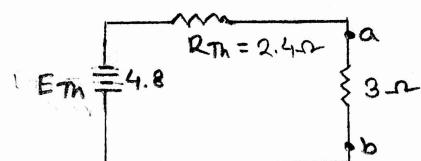

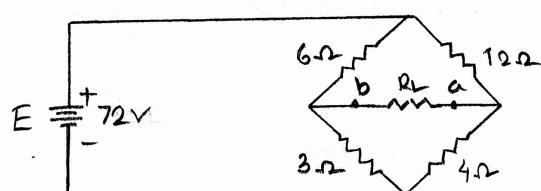Problem-22: Find the Thevenin equivalent circuit at terminal a-b for the network shown in the Figure below.



Find E_{Th} , (Fig a)

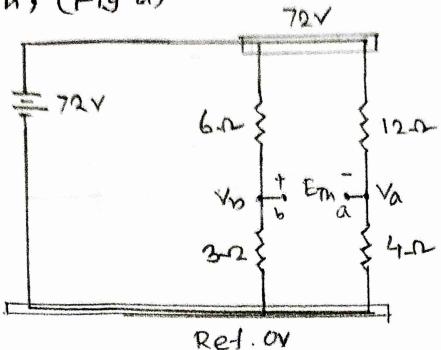


Fig : a

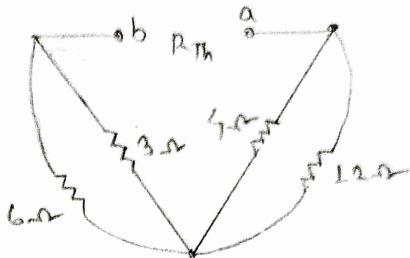


Fig : b

Applying KCL at node V_a ,

$$\frac{V_a - 72}{12} + \frac{V_a - 0}{4} = 0$$

$$\Rightarrow V_a - 72 + 3V_a = 0$$

$$\therefore V_a = 18 \text{ V}$$

Applying KCL at node V_b ,

$$\frac{V_b - 72}{6} + \frac{V_b - 0}{3} = 0$$

$$\Rightarrow V_b - 72 + 2V_b = 0$$

$$\Rightarrow V_b = 24 \text{ V}$$

$$\therefore E_{Th} = V_b - V_a = 24 - 18 = 6 \text{ V}$$

$$\begin{aligned} \therefore R_{Th} &= (6\Omega \parallel 3\Omega) + (4\Omega \parallel 12\Omega) \\ &= 2\Omega + 3\Omega = 5\Omega \end{aligned}$$


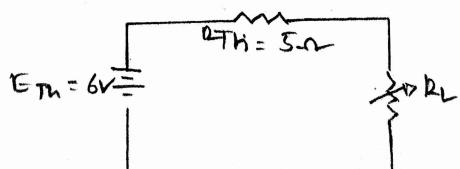


Fig: Thevenine equivalent circuit

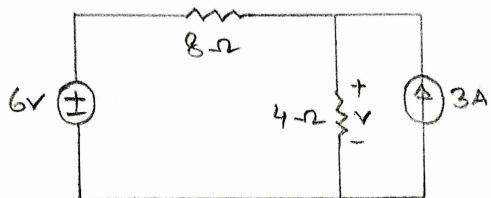Problem - 23: Use the superposition theorem to find v in the circuit of figure below.



Soln:

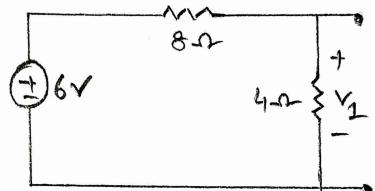


Fig (a)

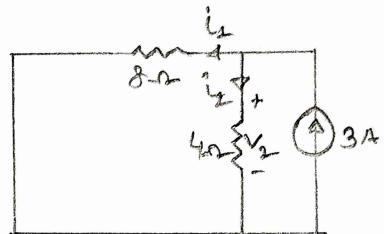


Fig (b)

Since there are two sources, let $v = v_1 + v_2$

To obtain v_1 we replace 3A current source by an open circuit

\therefore Applying VDR at fig (a),

$$v = \frac{4}{R_T} \cdot v_{\text{supply}} = \frac{4}{4+8} \times 6 = 2V$$

To obtain v_2 we replace 6V voltage source with a short circuit. Applying CDR at fig : b


$$\therefore i_2 = \frac{R_T}{4} \cdot I = \frac{2.67}{4} \times 3 = 2A$$

$$\therefore v_2 = i_2 \times 4 = 2 \times 4 = 8V$$

$$\therefore v = v_1 + v_2 = 2V + 8V = 10V$$

(Ans.)

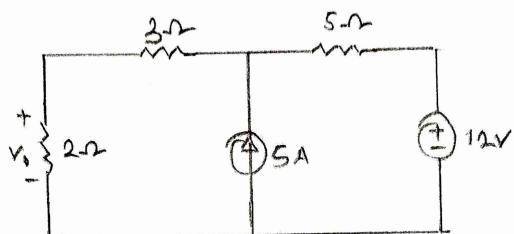Problem: 24 - Using superposition theorem, find v_o in the circuit of Figure below.



Solⁿ: Since there are two power source, let $v_o = v_1 + v_2$

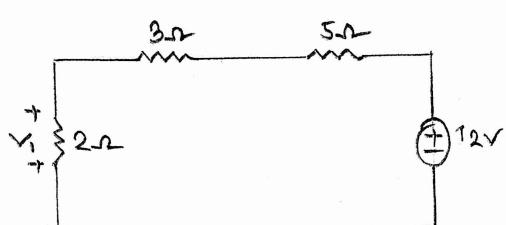


Fig: a

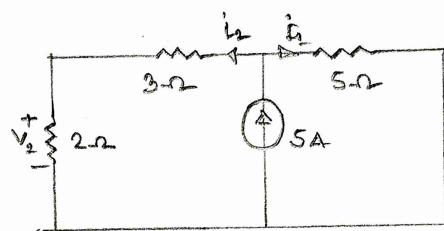


Fig: b

To obtain v_1 we replace 5A current source by an open circuit. Applying VDR at v_1 fig(a)

$$\therefore v_1 = \frac{2}{R_T} \cdot v_{\text{supply}} = \frac{2}{2+3+5} \times 12 = \frac{2}{10} \times 12 = 2.4 \text{ V}$$

To obtain v_2 we replace 12V voltage source by a short circuit. Applying CDR at (fig : b)


$$i_2 = \frac{R_T}{(2+3)} \cdot 5 = \frac{5}{5} \cdot 5 = 2.5 \text{ A}$$

$$\therefore v_2 = i_2 \times R_2 = 2.5 \times 2 = 5 \text{ V}$$

$$\therefore v_o = v_1 + v_2 = 2.4 + 5 = 7.4 \text{ V}$$

(Ans.)

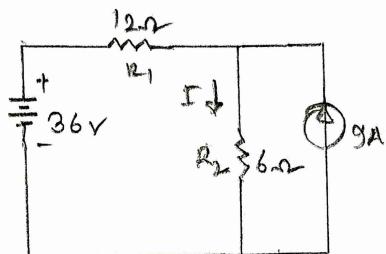PROBLEM : 25 - Using the superposition theorem determine the current through resistor R_2 for the network in figure below.



SOLⁿ: Since there are two power source let. $I = I_1 + I_2$

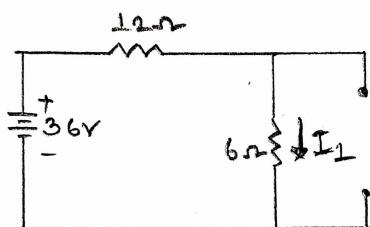


Fig : a

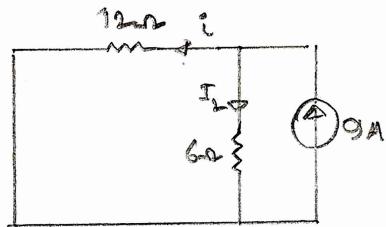


Fig : b

To obtain I_1 we replace 9A current source by an open circuit
Applying VDR at 6Ω resistor in fig : a

$$V_{6\Omega} = \frac{6}{6+12} \cdot 36 = 12V$$


$$\therefore I_1 = \frac{V_{6\Omega}}{6\Omega} = \frac{12}{6} = 2A$$

To obtain I_2 we replace 36V voltage source by a short circuit. Applying CDR at 6Ω resistor in fig : b

$$\therefore I_2 = \frac{R_T}{6} \cdot 9 = \frac{\left(\frac{1}{12} + \frac{1}{6}\right)^{-1}}{6} \cdot 9 = \frac{4}{6} \cdot 9 = 6A$$

\therefore current flow in R_2 resistor - $I = I_1 + I_2 = 2 + 6 = 8A$
(Ans.)

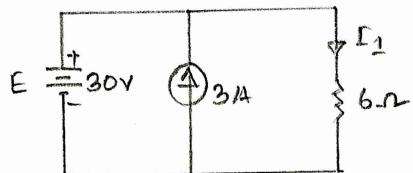Problem 26: Using the superposition theorem, determine current I_1 for the network in figure below.



Solⁿ: Since there is 2 power source, let $I_1 = i_a + i_b$

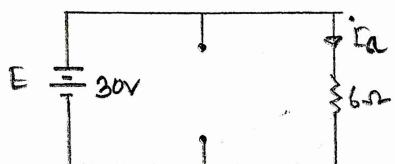


fig: a

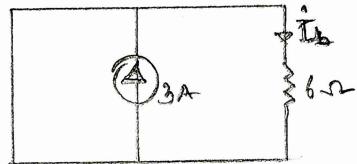


fig: b

current

To obtain i_a we replace 3A power source by an open circuit in fig(a)


$$\therefore i_a = \frac{E}{R} = \frac{30}{6} = 5A$$

To obtain i_b we replace 30V voltage source by a short circuit. As the circuit shorted there will be no current flow through 6 ohm resistor (Fig:b).

$$\therefore i_b = 0A$$

$$\therefore \text{current, } I_1 = i_a + i_b = 5 + 0 = 5A.$$

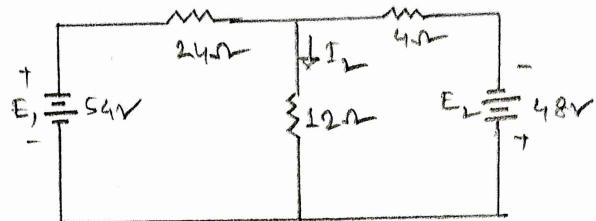Problem 27: Using the superposition theorem determine the current through 12Ω resistor in Figure below.



Solⁿ: Since there are 2 power source, Let $I_2 = i_{at} + i_b$

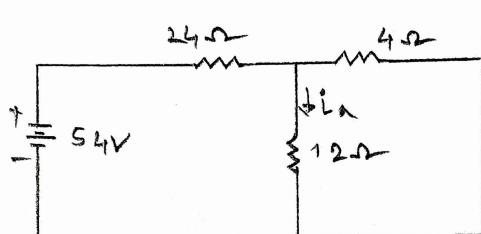


fig: a

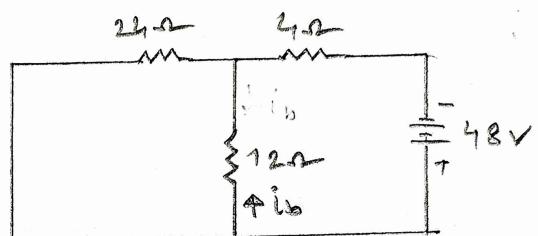


fig: b

To obtain i_a we replace 48V EMF source with an open circuit. (Fig: a). Applying VDR at 12Ω resistor,

$$V_{12\Omega} = \frac{\left(\frac{1}{12} + \frac{1}{4}\right)^{-1}}{R_T} E = \frac{3}{27} \times 54 = 6V$$

$$\therefore i_a = \frac{V_{12\Omega}}{12\Omega} = \frac{6}{12} = 0.5A$$

To obtain i_b we replace 54V EMF source with a short circuit (Fig: b) Applying VDR at 12Ω resistor.


$$V_{12\Omega} = \frac{\left(\frac{1}{12} + \frac{1}{24}\right)^{-1}}{\left(\left(\frac{1}{12} + \frac{1}{24}\right)^{-1} + 4\right)} \times 48 = 32V$$

$$\therefore i_b = \frac{V_{12\Omega}}{12} = \frac{32}{12} = 2.67A$$

$$\therefore I_2 = i_{at} + i_b \uparrow = i_b \uparrow - i_{at} = 2.67 - 0.5 = 2.17A \uparrow$$

(Ans)

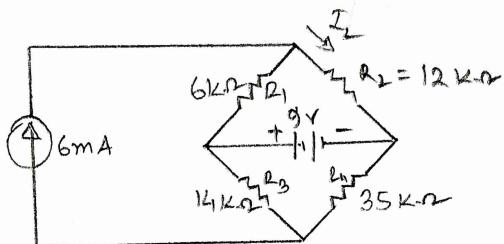Problem 28 : Using the principle of superposition theorem find the current I_2 through the $12\text{ k}\Omega$ resistor in Figure below



Solⁿ: since there is 2 power source let $I_2 = I_A + I_B$

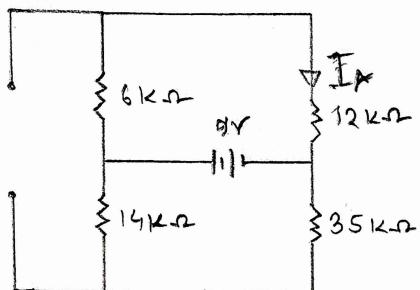


Fig:a

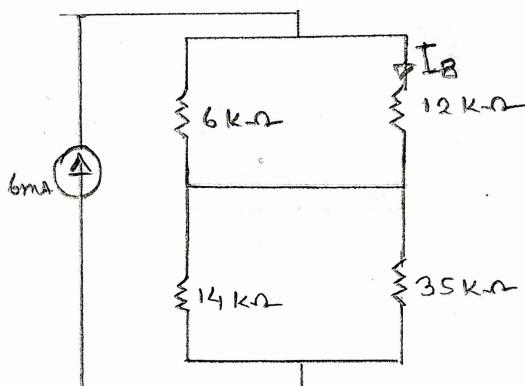


Fig:b

To determine I_A we replace 6mA current source with an open circuit (Fig:a).

as in parallel circuit voltage drop same and in series circuit current flow same.


$$I_A = \frac{9}{6+12} = 0.5 \text{ mA}$$

To determine I_B we replace 9V EMF source with a short circuit (Fig:b). Applying KDR at $12\text{k}\Omega$ resistor

$$\therefore I_B = \frac{12}{6+12} \cdot 6 = 2 \text{ mA}$$

\therefore current through $I_2 = I_A + I_B = 0.5 + 2 = 2.5 \text{ mA}$

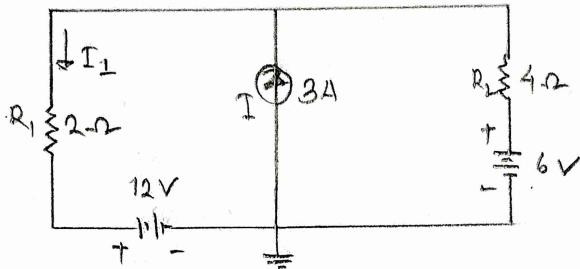Problem 29: Find the current through the 2Ω resistor of the network in figure below.



Soln: Since there are 3 power source, let $I_1 = I_A + I_B + I_C$

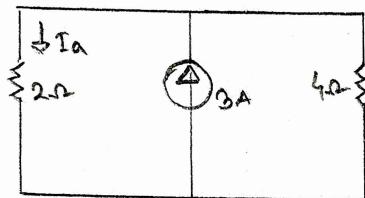


Fig: A

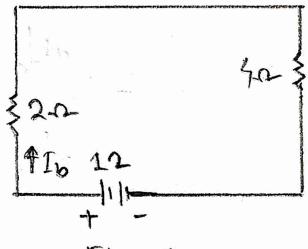


Fig: B

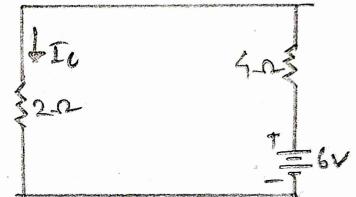


Fig: C

To determine I_A we replace 12V EMF source and 6V EMF source by short circuit. (Fig: A)

Applying CDR at 2Ω resistor,

$$I_A = \frac{R_T}{2\Omega} \times 3 = \frac{4}{2+4} \times 3 = 2A \downarrow$$

To determine I_B we replace 6V EMF source by short circuit and 3A current source by open circuit (Fig: B)

$$\therefore I_B = \frac{12V}{2\Omega + 4\Omega} = 2A \uparrow$$


To determine I_C we replace 12V EMF source by short circuit and 3A current source by open circuit (Fig: C)

$$\therefore I_C = \frac{6}{2+4} = 1A \downarrow$$

$$\therefore I_1 = I_A \downarrow + I_B \uparrow + I_C \downarrow = (I_A - I_B + I_C) \downarrow = 2 - 2 + 1 = 1A \downarrow$$

(Ans)

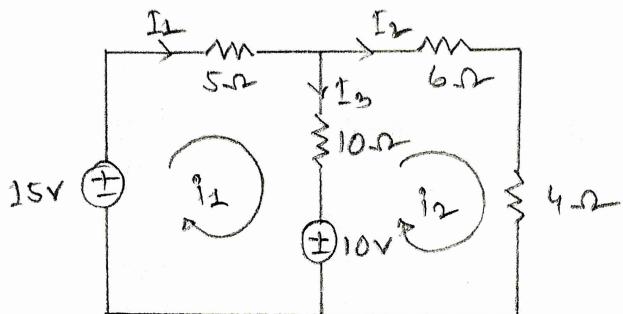Problem-30: For the circuit below find the branch currents I_1 , I_2 and I_3 using mesh analysis.



Solⁿ:

Applying KVL at mesh i_1 ,

$$5i_1 + 10(i_2 - i_1) + 10 - 15 = 0$$

$$\Rightarrow 15i_1 - 10i_2 = 5$$

$$\Rightarrow 3i_1 - 2i_2 = 1 \quad \text{--- (1)}$$

Applying KVL at mesh i_2 ,

$$6i_2 + 4i_2 - 10 + 10(i_2 - i_1) = 0$$

$$\Rightarrow 20i_2 - 10i_1 = 10$$

$$\Rightarrow 2i_2 - i_1 = 1 \quad \text{--- (2)}$$

$$\{(1)+(2)\} \Rightarrow 3i_1 - 2i_2 + 2i_2 - i_1 = 1+1$$

$$\Rightarrow 2i_1 = 2$$

$$\therefore i_1 = 1A \therefore i_2 = 1A.$$


$$\therefore I_1 = 1A$$

$$\therefore I_2 = 1A$$

$$\therefore I_3 = i_1 - i_2 = 1 - 1 = 0A$$

(Ans)

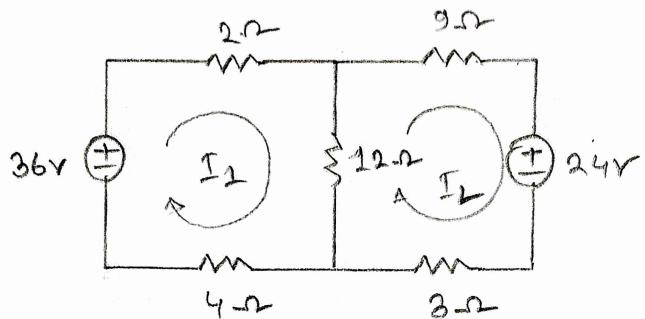Problem-31: calculate the mesh current I_1 and I_2 of the circuit below.



Soln:

Applying KVL at mesh I_1 ,

$$2I_1 + 12(I_1 + I_2) + 4I_1 - 36 = 0$$

$$\Rightarrow 18I_1 + 12I_2 = 36$$

$$\Rightarrow 3I_1 + 2I_2 = 6 \quad \text{--- (1)}$$

Applying KVL at mesh I_2 ,

$$9I_2 + 24 + 3I_2 + 12(I_2 - I_1) = 0$$

$$\Rightarrow 24I_2 - 12I_1 = -24$$

$$\Rightarrow 2I_2 - I_1 = -2 \quad \text{--- (2)}$$

$$\{(1) - (2)\} \Rightarrow 3I_1 + 2I_2 - 2I_2 + I_1 = 6 + 2$$


$$\Rightarrow 4I_1 = 8$$

$$\therefore I_1 = 2 \text{ A.}$$

$$\therefore I_2 = (-2 + I_1)/2 = 0 \text{ A.}$$

(Ans.)

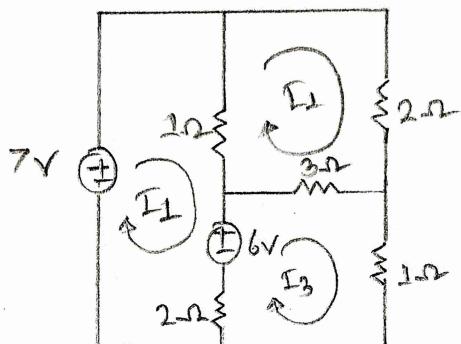□ Problem - 34: Use mesh analysis to determine the three mesh currents in the circuit below.



Solⁿ:

Applying KVL at mesh I_1 ,

$$(I_1 - I_2) + 6 + 2(I_2 - I_3) - 7 = 0$$

$$\Rightarrow I_1 - I_2 + 2I_2 - 2I_3 = 1$$

$$\Rightarrow 3I_2 - I_2 - 2I_3 = 1 \quad \text{--- (1)}$$

Applying KVL at mesh I_2 ,

$$2I_2 + 3(I_2 - I_3) + (I_2 - I_1) = 0$$

$$\Rightarrow 2I_2 + 3I_2 - 3I_3 + I_2 - I_1 = 0$$

$$\Rightarrow -I_1 + 6I_2 - 3I_3 = 0 \quad \text{--- (2)}$$

Applying KVL at mesh I_3 ,

$$3(I_3 - I_2) + I_3 + 2(I_3 - I_1) - 6 = 0$$

$$\Rightarrow 3I_3 - I_2 + I_3 + 2I_3 - 2I_1 - 6 = 0$$

$$\Rightarrow -2I_1 - 3I_2 + 6I_3 = 6 \quad \text{--- (3)}$$


By solving equation 1, 2, 3

$$I_2 = 3A$$

$$I_1 = 2A$$

$$I_3 = 3A$$

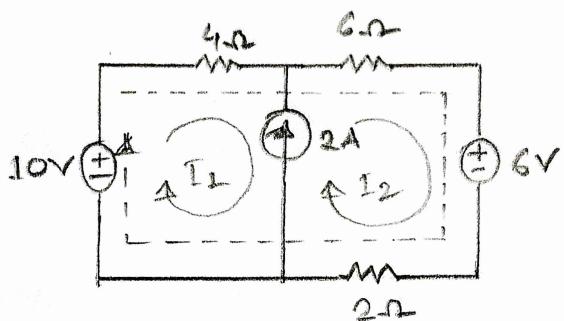■ Problem 36 - In the circuit shown in figure below determine the current through 2Ω resistor.



Applying KVL at supermesh,

$$4I_2 - 10 + 6I_2 + 6 + 2I_2 = 0$$

$$\Rightarrow 4I_2 + 8I_2 = 4$$

$$\Rightarrow I_2 + 2I_2 = 1 \quad \text{--- (1)}$$

$$\therefore I_2 - I_1 = 2 \quad \text{--- (2)}$$


$$\{ (1) + (2) \} \Rightarrow I_1 + 2I_2 + I_2 - I_1 = 1 + 2$$

$$\Rightarrow 3I_2 = 3$$

$$\therefore I_2 = 1A$$

$$\therefore I_1 = I_2 - 2 = 1 - 2 = -1A \quad (\text{Ans.})$$

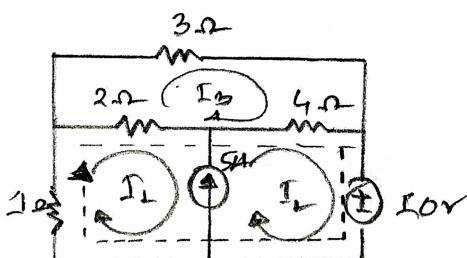■ Problem 37 - In the circuit shown below determine all the loop currents.



Applying KVL at supermesh.

$$I_1 + 2(I_1 - I_3) + 4(I_2 - I_3) + 10 = 0$$

$$\Rightarrow 3I_1 + 4I_2 - 6I_3 = -10 \quad \text{--- (1)}$$

$$I_2 - I_1 = 5 \quad \text{---} \quad (2)$$

Applying KVL at mesh I_3 ,

$$3I_3 + 4(I_3 - I_2) + 2(I_3 - I_1) = 0$$

$$\Rightarrow 3I_3 + 4I_3 - 4I_2 + 2I_3 - 2I_1 = 0$$

$$\Rightarrow -2I_3 - 4I_2 + 9I_3 = 0$$

Solving the above equations,


$$I_1 = -5.5556 \text{ A}$$

$$I_2 = -0.5556 \text{ A}$$

$$I_3 = -1.4815 \text{ A}$$

(Ans.)

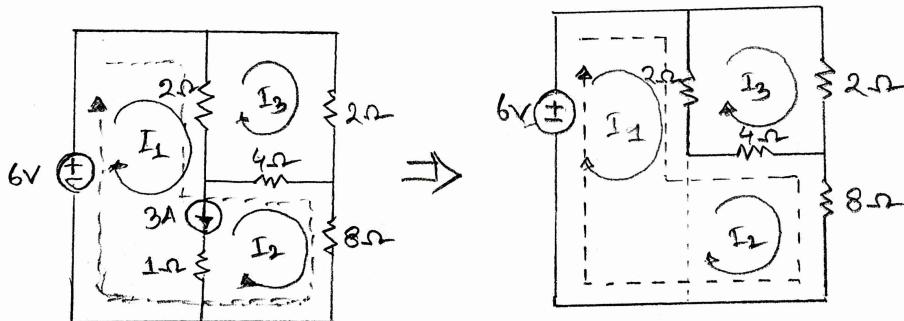Problem: 38 - Use mesh analysis to determine all the mesh currents in the figure below.



Applying KVL at supermesh,

$$2(I_2 - I_3) + 4(I_2 - I_1) + 8I_2 - 6 = 0$$

$$\Rightarrow 2I_1 - 2I_3 + 4I_2 - 4I_1 + 8I_2 - 6 = 0$$

$$\Rightarrow 2I_1 + 12I_2 - 6I_3 = 6 \quad \text{---} \quad (1)$$

$$\therefore I_1 - I_2 = 3 \quad \text{---} \quad (2)$$

Applying KVL at mesh I_3 ,

$$2I_3 + 4(I_3 - I_2) + 2(I_3 - I_1) = 0$$

$$\Rightarrow 2I_3 + 4I_3 - 4I_2 + 2I_3 - 2I_1 = 0$$

$$\Rightarrow -2I_1 - 4I_2 + 8I_3 = 0 \quad \text{--- (3)}$$


By solving equation ①; ②; ③,

$$I_1 = 3.4737 \text{ A}$$

$$I_2 = 0.4736 \text{ A}$$

$$I_3 = 1.1052 \text{ A} \quad (\text{Ans.})$$

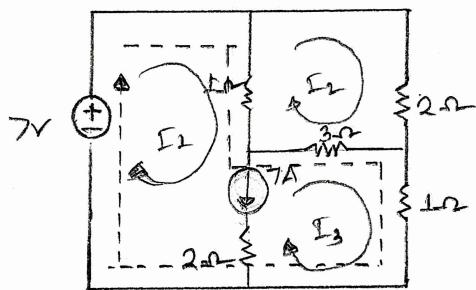Problem - 39: Determine the three mesh current in figure below.



Applying KVL at supermesh

$$I_1 - I_2 + 3(I_2 - I_3) + I_3 - 7 = 0$$

$$\Rightarrow I_1 - I_2 + 3I_2 - 3I_3 + I_3 - 7 = 0$$

$$\Rightarrow I_1 - 4I_2 + 4I_3 = 7 \quad \text{--- (1)}$$

$$I_1 - I_3 = 7 \quad \text{--- (2)}$$

Applying KVL at mesh I2,


$$2I_2 + 3(I_2 - I_3) + I_2 - I_1 = 0$$

$$\Rightarrow -I_1 + 6I_2 - 3I_3 = 0 \quad \text{--- (3)}$$

By solving above equations,

$$I_1 = 9 \text{ A}, I_2 = 2.5 \text{ A}, I_3 = 2 \text{ A} \quad (\text{Ans.})$$

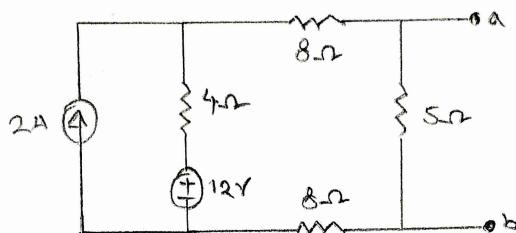Problem - 40: Find the norton equivalent circuit of the circuit in the Figure shown below.



Soln:

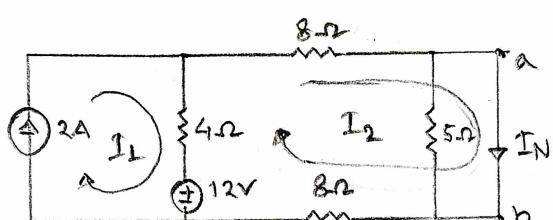


Fig:a

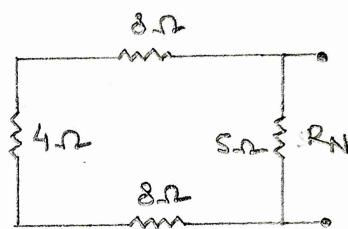


Fig:b

Find I_N (Fig:a)

Applying KVL in I_2 mesh,

$$4(I_2 - I_1) + 8I_2 + 8I_2 - 12 = 0$$

$$\Rightarrow -4I_1 + 20I_2 = 12$$

$$\Rightarrow -4 \times 2 + 20I_2 = 12$$

$$\Rightarrow I_2 = \frac{12}{20} = 1A$$

$$\therefore I_N = I_2 = 1A$$


From mesh I_1 ,
 $I_1 = 2A$

Find R_N (Fig:b)


$$R_N = (8\Omega + 4\Omega + 8\Omega) // 5\Omega$$

$$= 20\Omega // 5\Omega = 4\Omega$$

\therefore Norton Equivalent circuit:

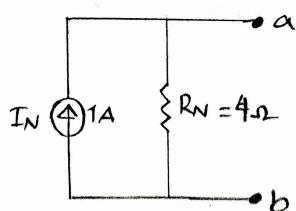

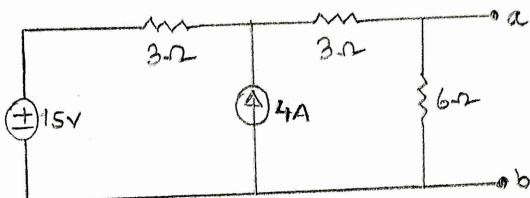Problem 41: Find the Norton equivalent circuit for the circuit in figure below at terminal a-b.



Soln:

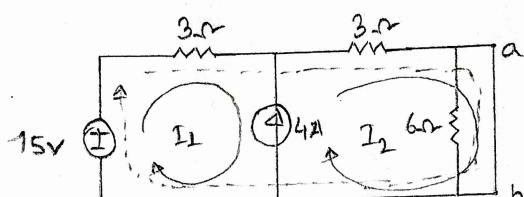


Fig : a

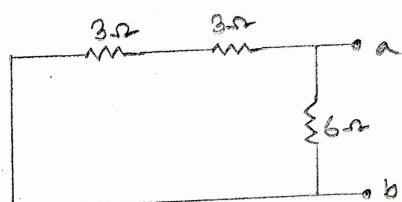


Fig: b

Find I_N (Fig:a)

Applying KVL at ^{super} mesh I_1 ,

$$3I_1 + 3I_2 - 15 = 0$$

$$\therefore I_1 + I_2 = 5 \quad \text{--- (1)}$$

$$\therefore I_2 - I_1 = 4 \quad \text{--- (2)}$$

Solving equation (1) and (2)

$$I_1 = 0.5 \text{ A}$$

$$I_2 = 4.5 \text{ A}$$


$$\therefore I_N = I_2 = 4.5 \text{ A}$$

Find R_N (Fig:b)


$$R_N = (3\Omega + 3\Omega) \parallel 6\Omega$$

$$= 3\Omega$$

\therefore Norton Equivalent circuit:

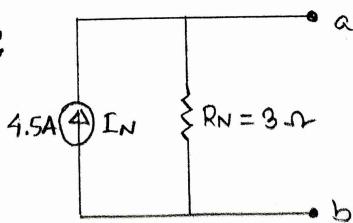

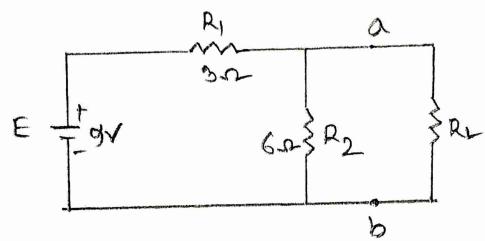Problem 42: Find the norton equivalent circuit for the network in the circuit below for point a-b.



SOLN:

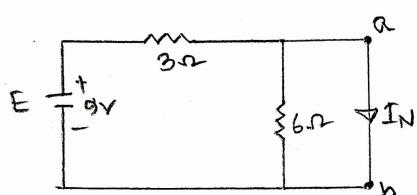


Fig: a

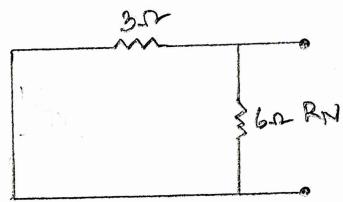


Fig: b

Find I_N (Fig: a)


As this circuit shorted the current will only flow through 3Ω resistor.

$$\therefore I_N = \frac{9}{3} = 3A$$


Find R_N (Fig: b)

$$\therefore R_N = 3\Omega // 6\Omega = 2\Omega$$

\therefore Norton Equivalent circuit:

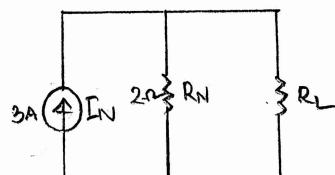

Problem 43: Find the Norton equivalent circuit for the network in point a-b to the 9Ω resistor.

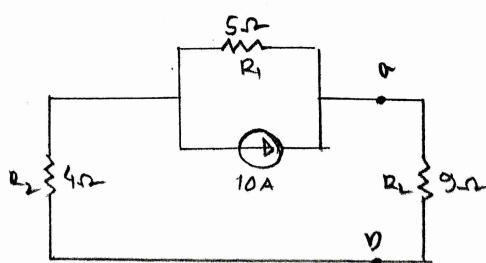

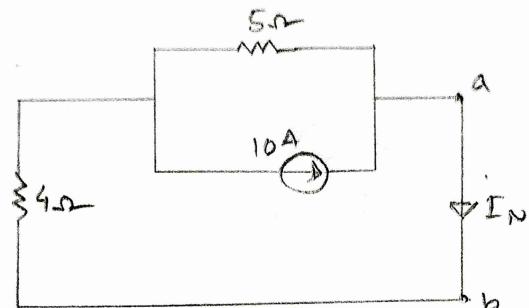


Fig: a

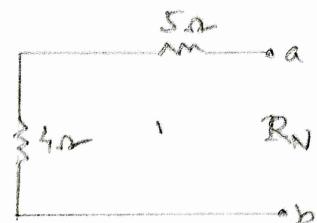


Fig: b

Find I_N (Fig: a)


Applying KCL at 4Ω resistor,

$$I_N = \frac{\left(\frac{1}{4} + \frac{1}{5}\right)^{-1}}{4} \cdot 10 = 5.556 \text{ A}$$


Find R_N (Fig: b)

$$R_N = 5\Omega + 4\Omega = 9\Omega$$


∴ Norton Equivalent circuit:

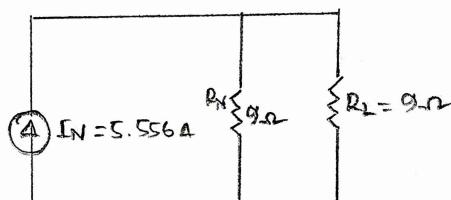

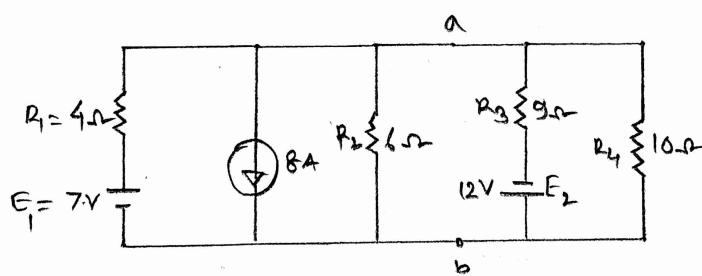Problem 44: Find the Norton equivalent circuit for the portion of network of a-b in the figure below.




Solⁿ:

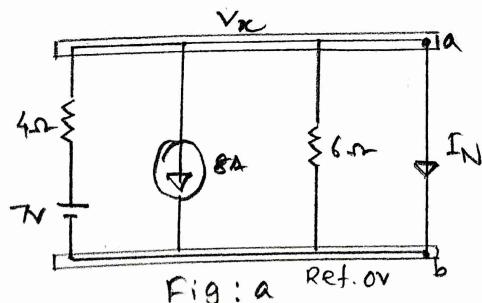

Find R_N (Fig: b)

$$R_N = 4\Omega || 6\Omega = 2.4\Omega$$

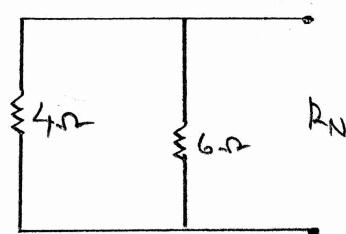

Find I_N (Fig: a)

Applying KCL at node V_N ,


$$\frac{V_N - 7}{4} + 8 = 0$$

$$\Rightarrow V_N + 25 = 0$$


$$\Rightarrow V_N = -25$$

$$\therefore I_N = \frac{V_N}{R_T} = \frac{-25}{4} = -6.25A$$

∴ Norton equivalent circuit :

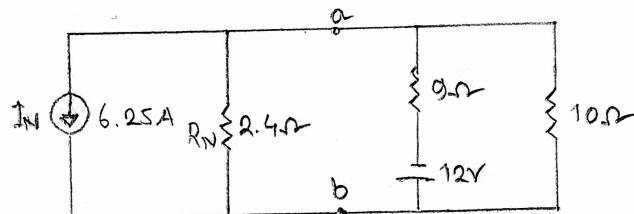

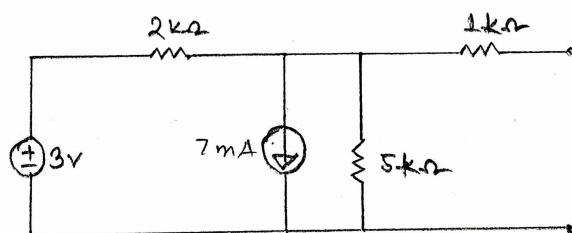PROBLEM: 45 - Determine the Thevenine and Norton Equivalents of the circuit below.



SOLⁿ:

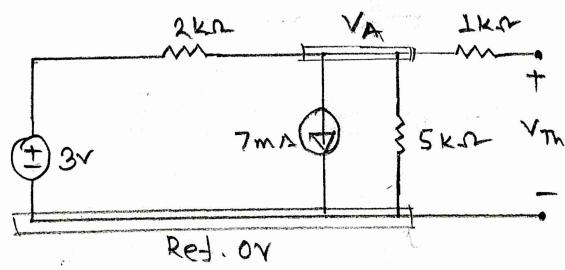


Fig: a

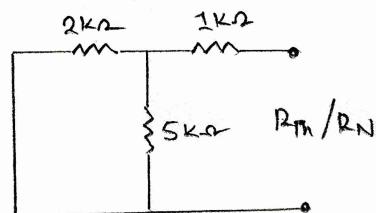


Fig: b

Find R_m / R_N : (Fig b)

$$R_m = R_N = (2k\Omega || 5k\Omega) + 1k\Omega = 2.429k\Omega$$

Find V_{Th} (Fig:a)

Applying KCL at Node V_A ,

$$\frac{V_A - 3}{2} + 7 + \frac{V_A - 0}{5} = 0$$

$$\therefore 5V_A - 15 + 70 + 2V_A = 0$$

$$\therefore 7V_A = -55$$



$$\therefore V_A = -7.857 \text{ V}$$

$$\therefore V_{Th} = V_A - 0 = -7.857 \text{ V}$$


We know,

$$I_N = \frac{V_{Th}}{R_{Th}} = -\frac{7.857}{2.429} = -3.235 \text{ mA}$$

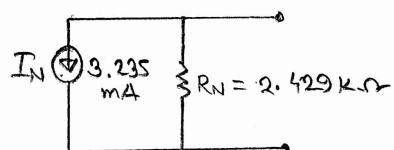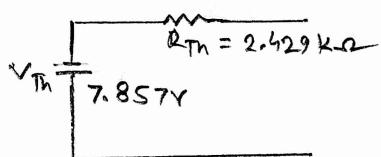∴ Thevenine and Norton Equivalent circuit:



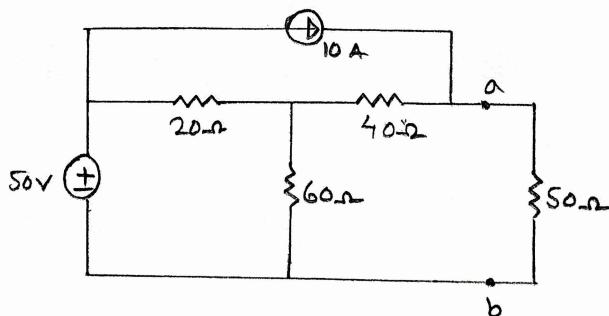Problem: 46 Find the norton equivalent circuit to a-b point/terminal in the shown figure below. Find the current through 50Ω resistor.



Solⁿ:

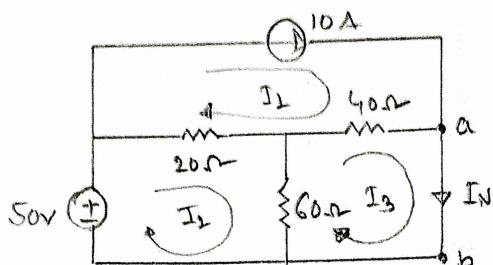


Fig: a

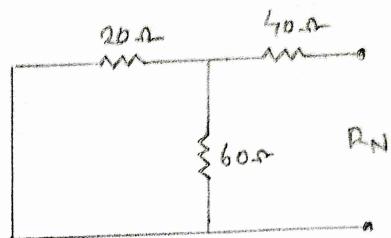


Fig: b

Finding I_N (Fig: a)

Applying KVL at mesh I_1 ,

$$I_L = 10 \text{ A}$$

Applying KVL at mesh I_2 ,

$$20(I_2 - I_1) + 60(I_2 - I_3) - 50 = 0$$

$$\Rightarrow 20I_2 - 20I_1 + 60I_2 - 60I_3 - 50 = 0$$

$$\Rightarrow 80I_2 - 60I_3 = 250$$

$$\Rightarrow 8I_2 - 6I_3 = 25 \quad \text{--- (1)}$$

Hence,
 $I_1 = 10 \text{ A}$

Applying KVL at mesh I_3 ,

$$40(I_3 - I_1) + 60(I_3 - I_2) = 0$$

$$\Rightarrow 40I_3 - 40I_1 + 60I_3 - 60I_2 = 0$$

$$\Rightarrow -60I_2 + 100I_3 = 400$$

$$\Rightarrow -6I_2 + 10I_3 = 40 \quad \text{--- (2)}$$

By solving equation (1) and (2)

$$I_2 = 11.136 \text{ A}$$


$$I_3 = 10.682 \text{ A}$$

$$\therefore I_N = I_3 = 10.682 \approx 10.7 \text{ A}$$

Finding R_N (Fig: b)

$$R_N = (20 \Omega || 60 \Omega) + 40 \Omega = 15 \Omega + 40 \Omega = 55 \Omega$$

∴ Norton Equivalent circuit:

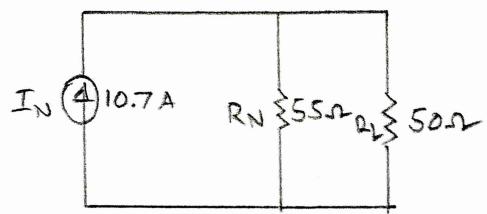

$$\therefore I_{R_L} = \frac{55}{55+50} \times 10.7 = 5.6 \text{ A}$$

(Ans.)